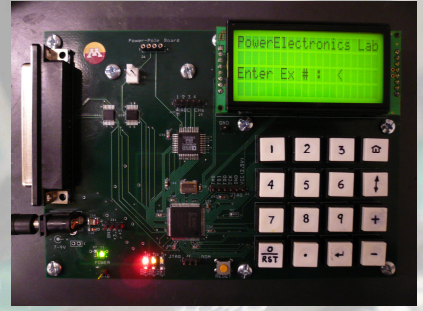


# ONR-Funded FPGA-Based Additional Experiments in the Power Electronics Lab

## FPGA Board




## FPGA-based Control Board

- Xilinx Spartan 3E FPGA
- User input with 16 push buttons
- User feedback with LCD Display
- Interface to Power-Pole Board as well as Drives Board
- On board 12-bit parallel ADC
- On board ROM - Completely stand-alone
- JTAG capable
- Single power supply
- Programmed with Verilog


## List of Experiments

- Open-Loop DC-DC Converters
- Feedback Control of DC-DC Converters
- PWM Control of Full-Bridge Converters
- Phase-Shift-Modulated Full-Bridge Converters
- Soft Switching
- Single-Phase AC Converters
- Three-Phase AC Converters


## Control of Buck Converter

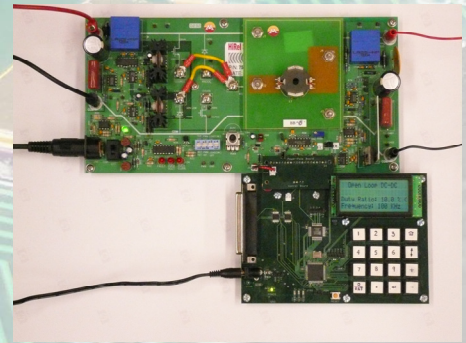


## Control of Full-Bridge Converter

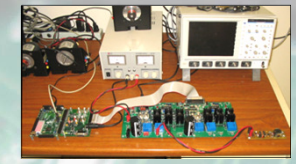

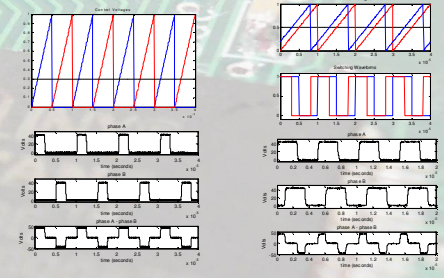
- Uses 2 of 3 inverter legs
- Secondary circuit includes transformer, rectifier and filter
- Switching technique - Pulse Width Modulation or Phase Shift Modulation




## Control of AC-Motor Drive

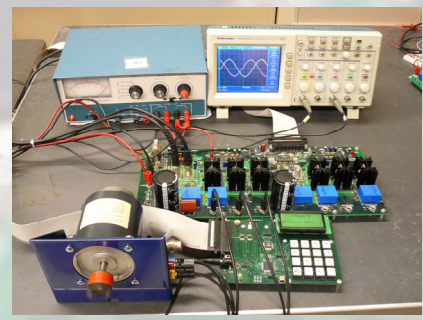


- Uses 3 inverter legs
- V/f control

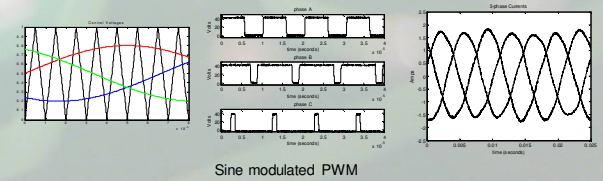


## Drives Board Control

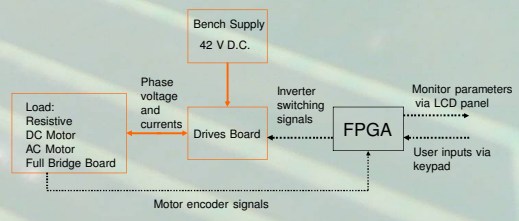


## Feedback Control

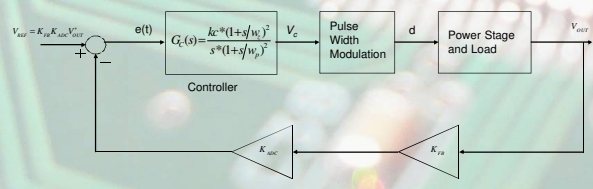

## Power Electronics Board Control

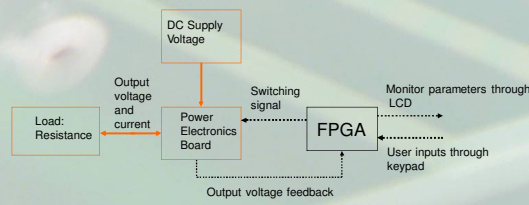

## Regulated Output Voltage

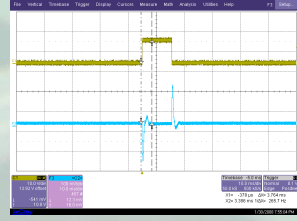

## Inductor Current



Sine modulated PWM