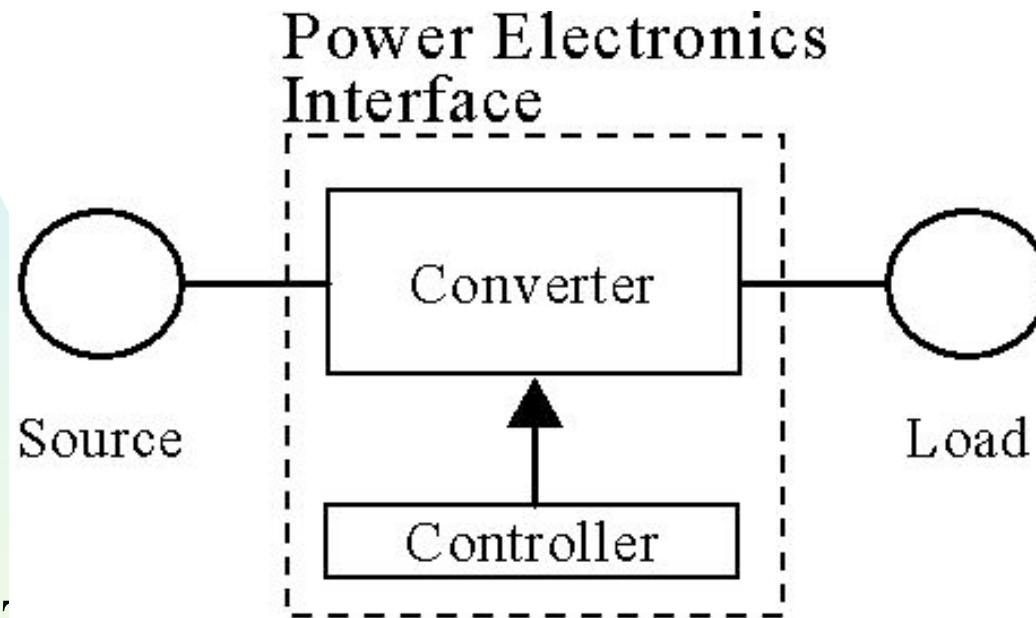


Course in Power Electronics





DC \Leftrightarrow DC

DC \Leftrightarrow AC

AC \Leftrightarrow Variable Frequency AC

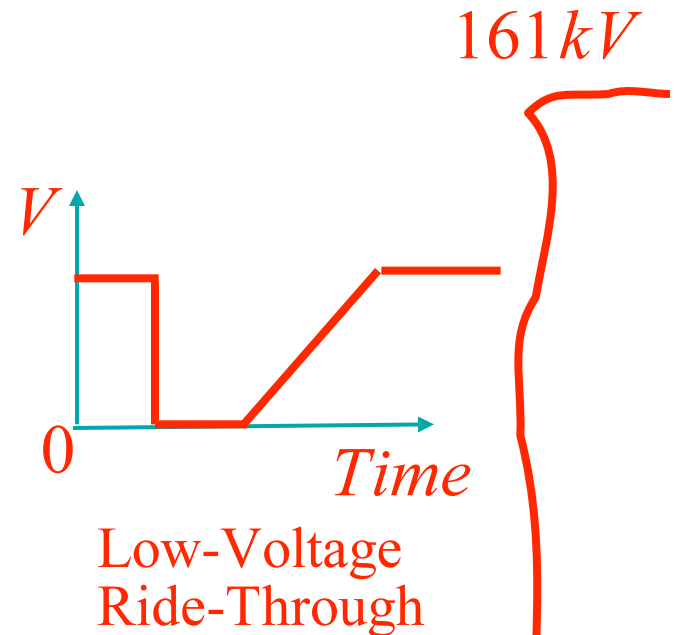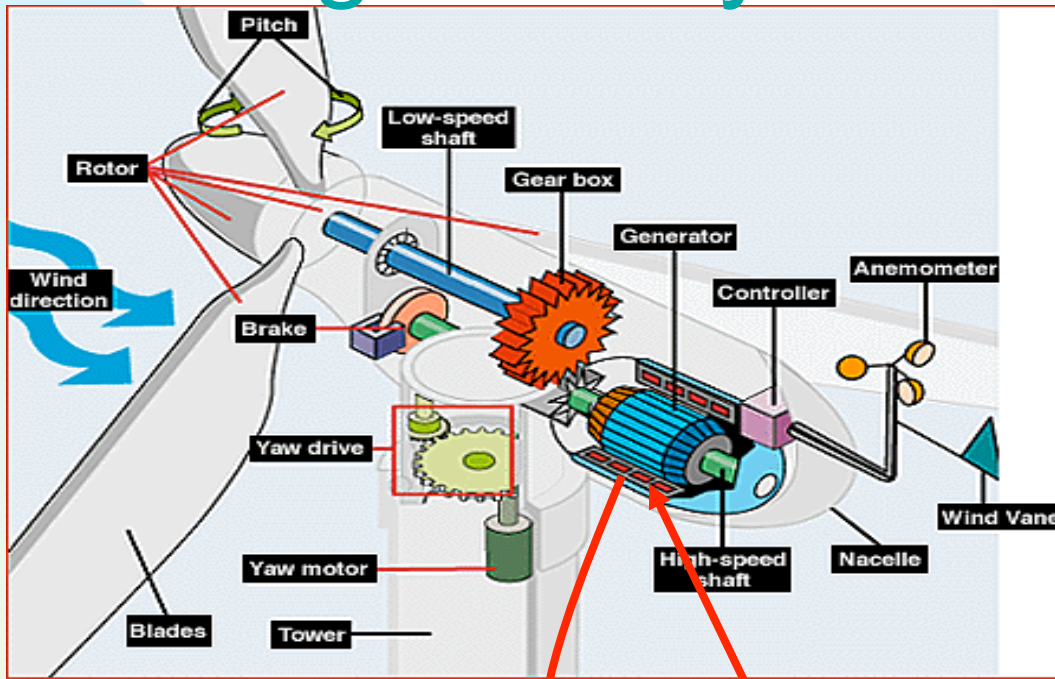
Windmills: Example of an Integrated System




$0 - 690\text{ V}$
 $10 - 60\text{ Hz}$

Generator

Power Electronics
Converters

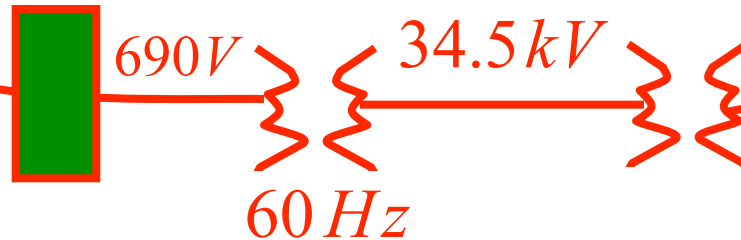


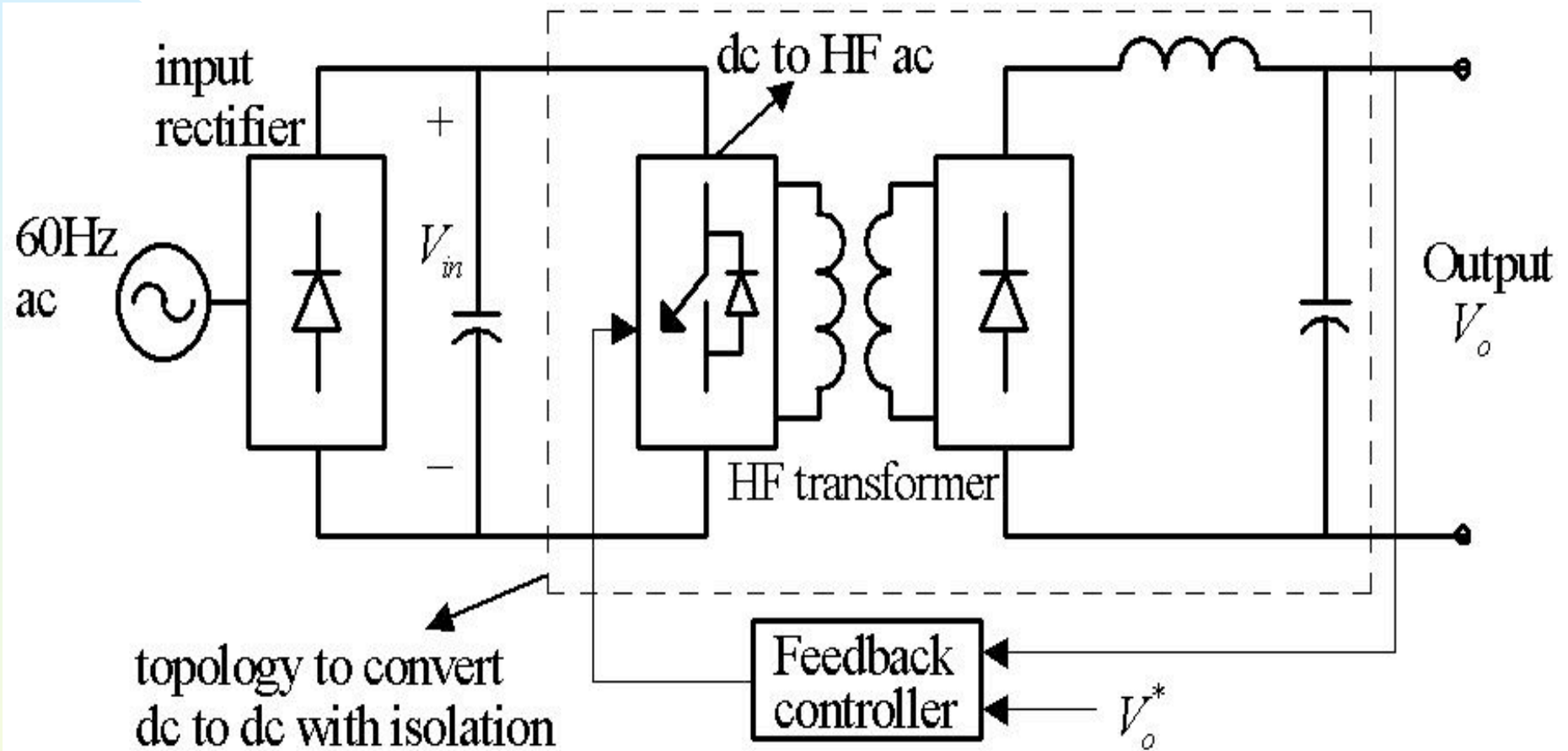Another Example : Switch-Mode DC Power Supply



High Efficiency is very important:

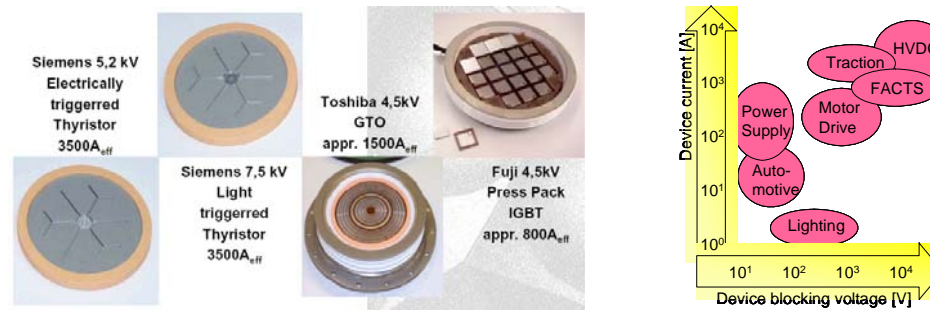
- Diodes, Thyristors, MOSFETs, IGBTs, GTOs, etc used as Switches



Beyond Silicon: New Materials


Key Parameters:

	Si	4H-SiC	Diamond
Bandgap	1.1	3	5 eV
Breakdown field	0.3	3	10 MV/cm
Max electron velocity	1.0	2	3 10^7 cm/s
Thermal conductivity	1.5	5	20 W/cmK

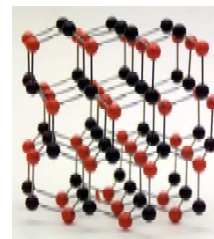



Silicon Carbide exceeds the fundamental limitations of Silicon by a factor 10-100 in improved device properties

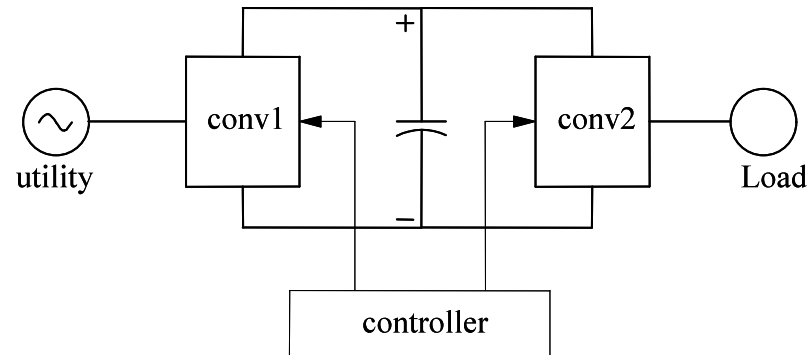A Common Topology: Voltage-Link Converters




Switching Power-Pole: Building-block of converters

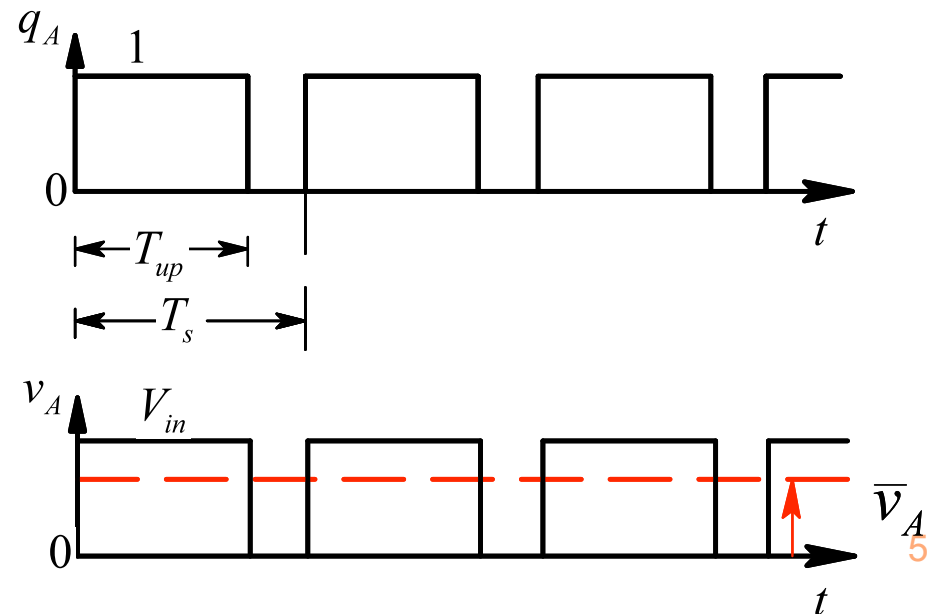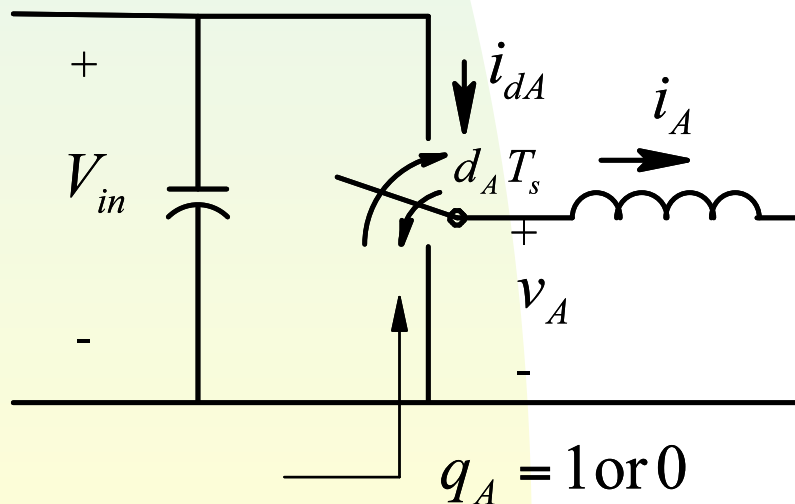
- Synthesis by Pulse-Width Modulation
- Bidirectional Power Flow



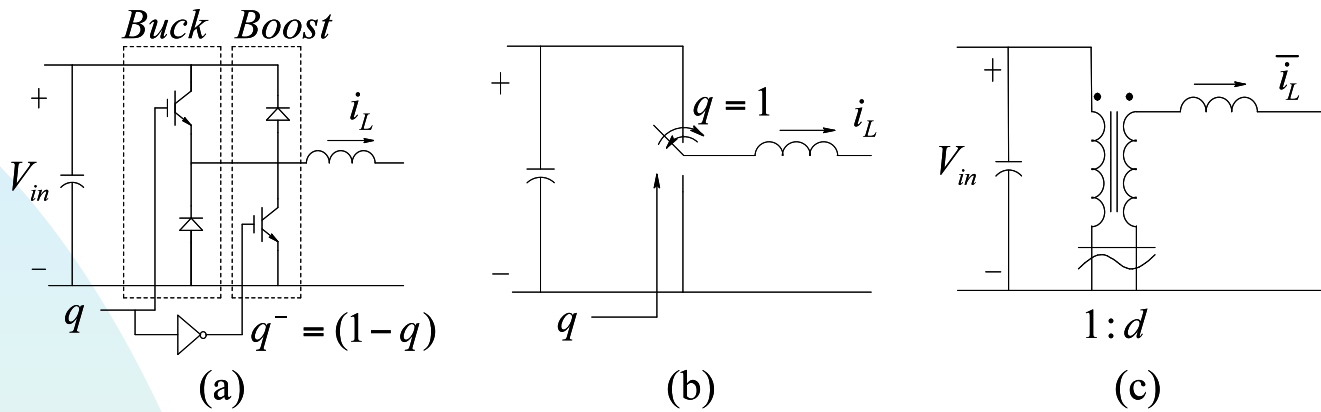
Average Representation of the Switching Power-Pole:




Feedback Control assisted by PSpice:

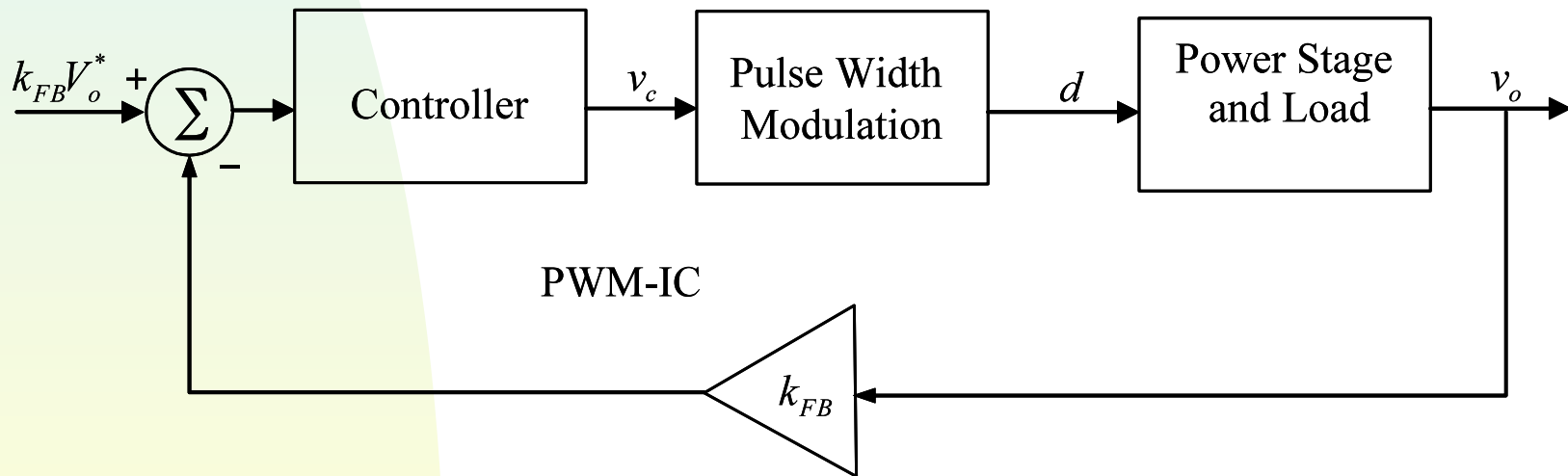

Converters for DC and AC Motor Drives:

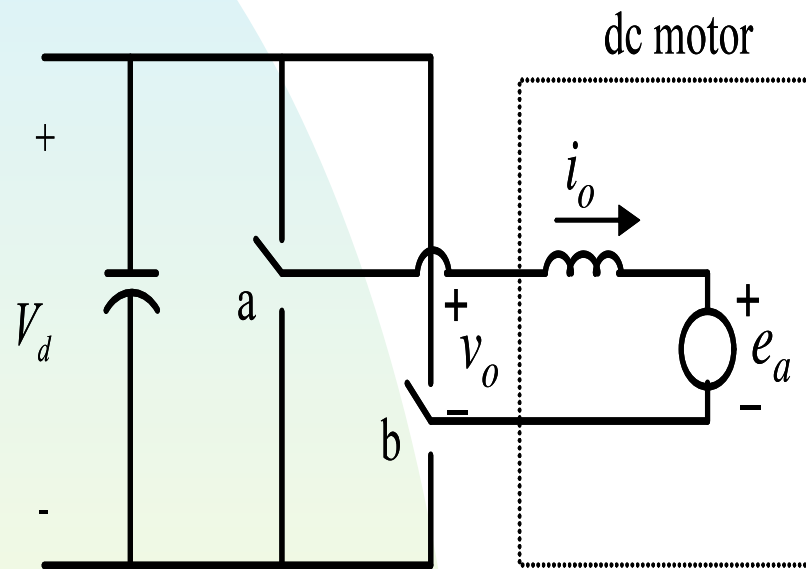

(a)

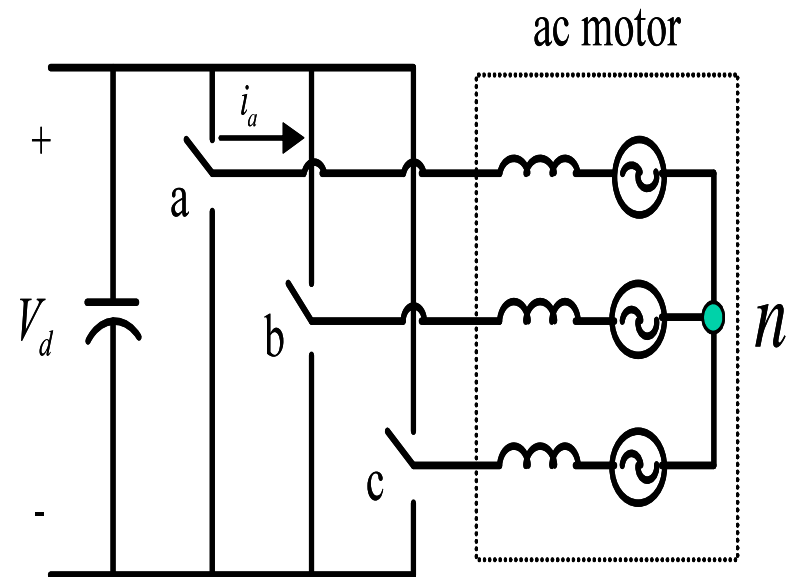

(b)

Topics Covered in this Course:

- Switch-Mode Converters
 - ◆ Buck, Boost, Buck-Boost
 - ◆ Flyback, Forward, Full-Bridge
 - ◆ DC and AC Motor Drives
 - ◆ Power-Factor-Correction Circuits
- Feedback Control
- Thyristor Converters

Textbook:

- Presentation Slides
- Solutions Manual





PSpice-based Lab:

(Using Student/Evaluation Version)


- Switching Power-Pole
- Capacitor Characteristic
- Buck, Boost, Buck-Boost Converters
- Average Modeling of dc-dc Converters
- Feedback Control: Voltage & Current-Mode
- Frequency Response in DCM
- Flyback, Forward and Full-Bridge Converters
- Soft-Switching in DC-DC Converters
- Converters for DC-Motor Drives
- Converters for 3-Phase AC Motor Drives
- Thyristor Converters

Hardware Lab: very low-cost

Switching Power - Pole Board

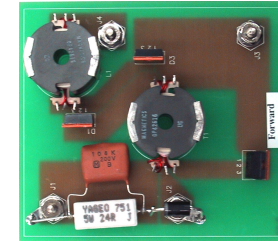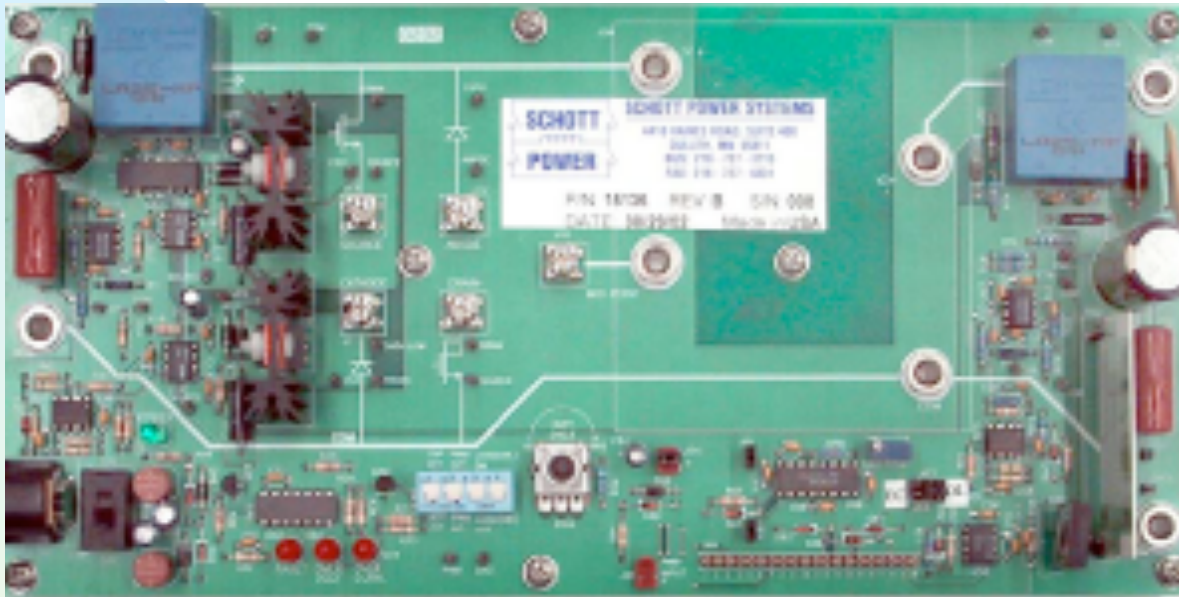

Magnetics Plug - In Board

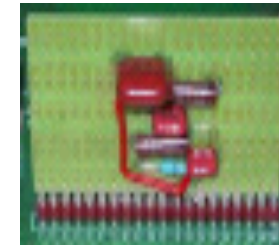

Feedback Control Plug - In Board

Power Electronics Laboratory

User Manual

**Department of Electrical and Computer
Engineering**

University of Minnesota


Revised: August 12, 2008

Experiments:


- Buck, Boost, Buck-Boost
- Feedback Control: Voltage-Mode, Peak-Current-Mode
- Flyback, Forward

Additional Experiments Using FPGAs (funded by ONR)

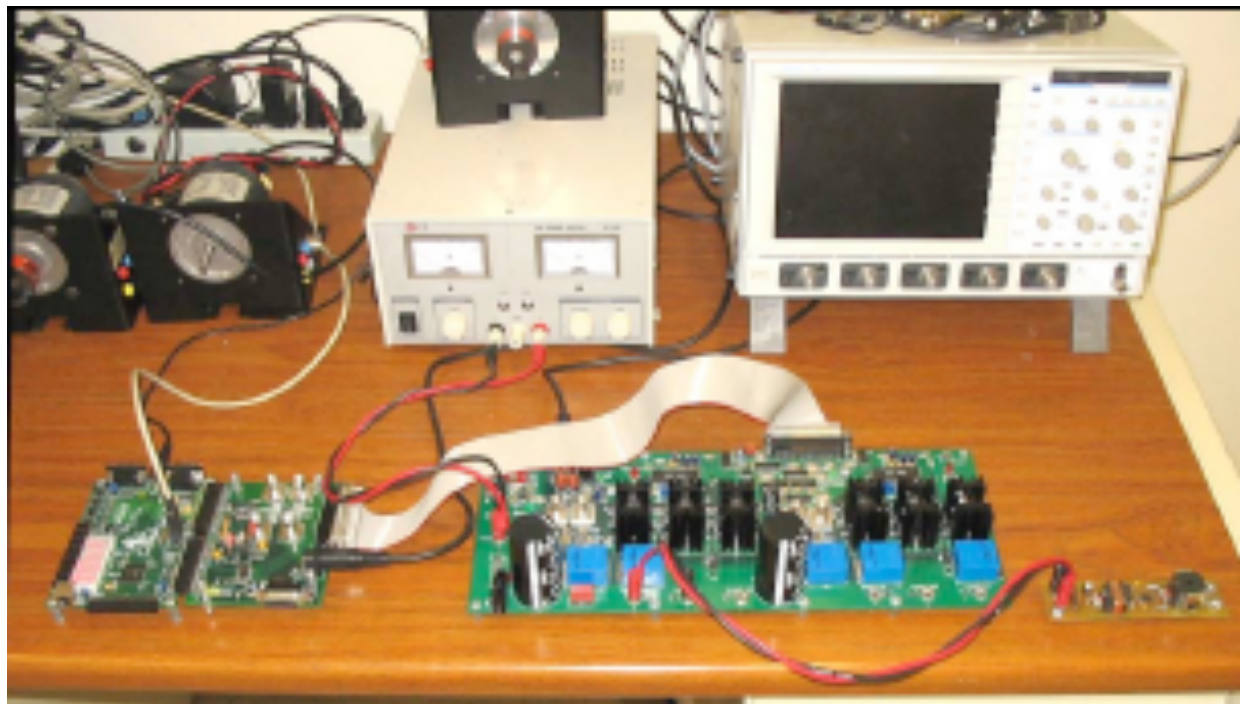- Digital Control of DC-DC Converters
- Full-Bridge DC-DC Converters
- Soft-Switching in Full-Bridge DC-DC Converters
- DC Motor Drives
- 3-Phase AC Drives



Hands-on Construction Kit:

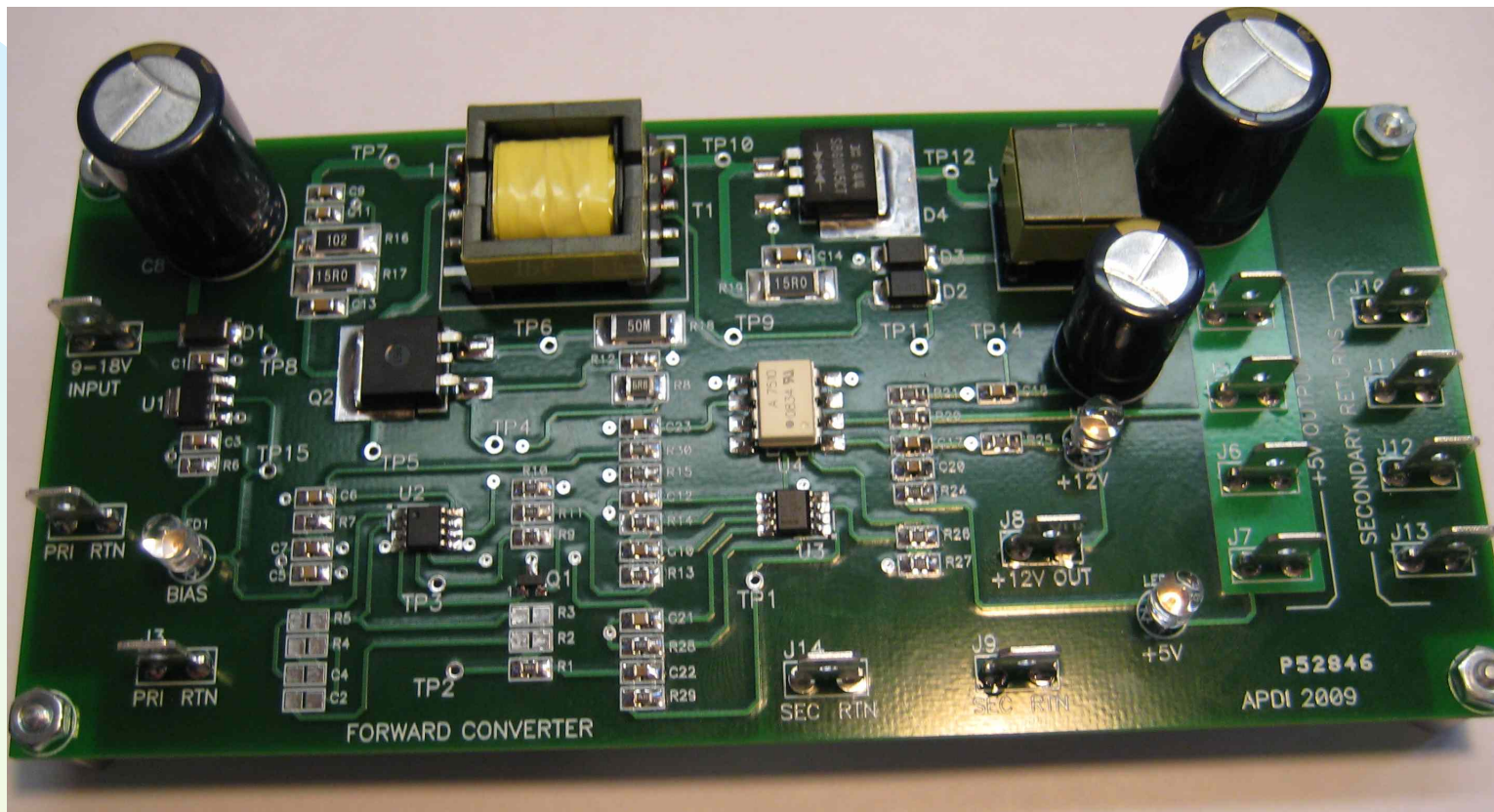

- Forward converter with regulated output
 - Components and circuit board provided.
 - Students mount (solder) components on board and test converter.

Graduate-Level Textbook:

