
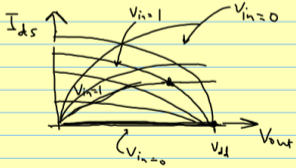
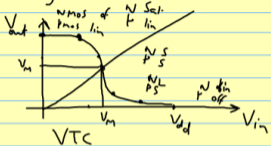


# Inverter Analysis

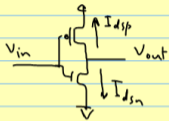

$V_m =$  switching threshold (trip point)

$$V_M$$

$$I_{dsn} = -I_{dsp}$$

$$\underbrace{\left(\mu \frac{C_{ox} W}{L}\right)_n}_{k_n} (V_M - V_{tn} - \frac{V_{dsatn}}{2}) \cdot V_{dsatn} = -k_p (V_M - V_{dd} - V_{tp} - \frac{V_{dsatp}}{2}) \cdot V_{dsatp}$$

$$V_M - V_{tn} - \frac{V_{dsatn}}{2} = \underbrace{\left(\frac{k_p V_{dsatp}}{k_n V_{dsatn}}\right)}_{r} \cdot (V_M - \dots)$$

$$V_M = \frac{V_{tn} + \frac{V_{dsatn}}{2} + r(V_{tp} + \frac{V_{dsatp}}{2} + V_{dd})}{1+r}$$

$$r \approx 1 \text{ and } V_{dd} \text{ large} \Rightarrow V_M \approx \frac{r}{1+r} V_{dd}$$