

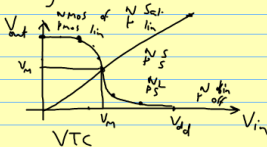


# Inverter Analysis

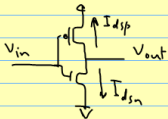

VTC  
(Voltage Transfer Curve)

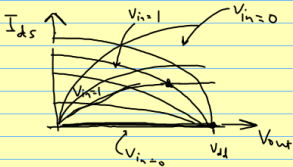

$V_m =$  switching threshold  
(trip point)

$$V_{in} = V_{out}$$

$$V_M$$

$$I_{dsn} = -I_{dsp}$$


$$\underbrace{\left(\mu \frac{C_{ox} W}{L}\right)}_n k_n (V_M - V_{tn} - \frac{V_{dsatn}}{2}) \cdot V_{dsatn} = -k_p (V_M - V_{dd} - V_{tp} - \frac{V_{dsatp}}{2}) \cdot V_{dsatp}$$

$$V_M - V_{tn} - \frac{V_{dsatn}}{2} = - \frac{k_p V_{dsatp}}{k_n V_{dsatn}} \cdot (V_M - \dots)$$

$$\underline{V_M} = \frac{V_{tn} + \frac{V_{dsatn}}{2} + r(V_{tp} + \frac{V_{dsatp}}{2} + V_{dd})}{1+r}$$

$$\underline{r \approx 1} \text{ and } V_{dd} \text{ large} \Rightarrow \underline{V_M} \approx \frac{r}{1+r} V_{dd}$$

# [Design Steps]



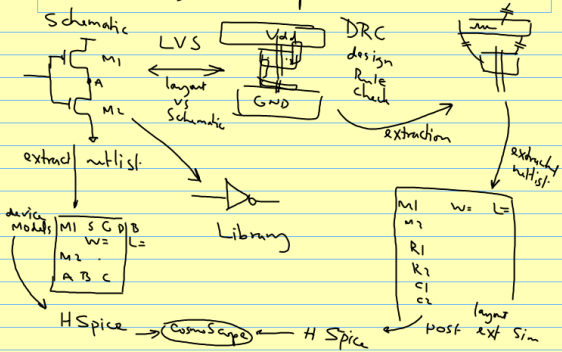


$$V_M \quad \text{and} \quad r=1 \quad \left( \begin{array}{l} \text{b/c want} \\ V_M = \frac{1}{2} V_{DD} \end{array} \right)$$

$$r = \frac{k_p V_{dsatp}}{k_n V_{dsatn}} = \frac{\left( \cancel{\mu_{ox}} \frac{W}{L} \right)_p}{\left( \cancel{\mu_{ox}} \frac{W}{L} \right)_n} \cdot \frac{V_{dsatp}}{V_{dsatn}} = 1$$


$$\frac{W_p}{W_n} = \frac{\mu_n}{\mu_p} \cdot \frac{\cancel{V_{dsatp}}}{\cancel{V_{dsatn}}} \approx 2$$

# NOISE vs Speed

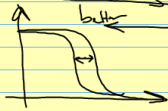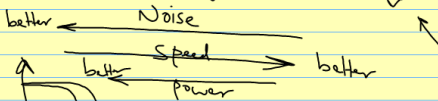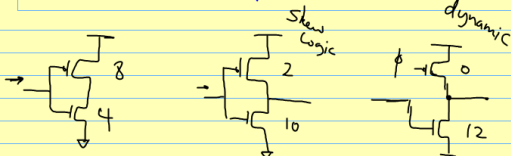

$$\text{delay} \propto \frac{1}{w}$$

# NOISE Margin

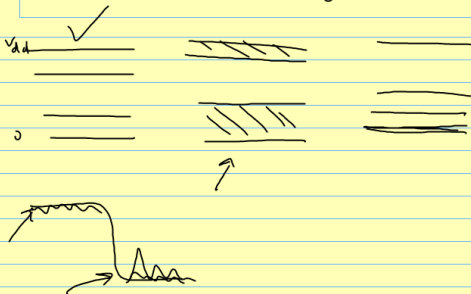

# Regenerative Property

