
 


## Combinational vs. Sequential Logic

 

Combinational


$$\text{Output} = f(\text{In})$$



Sequential

$$\text{Output} = f(\text{In}, \text{Previous In})$$

# Static Complementary CMOS

 




PUN and PDN are **dual** logic networks

# Combinational Logic ch6




Static CMOS

— PUN and PDN EXCLUSIVE


⇒ out conn EITHER  $V_{dd}$  or GND

   

# Logic Gates

   

$$\overline{A \cdot B}$$

 


$$\overline{A+B}$$




$$\overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A+B}}$$
 
$$\overline{\overline{A+B}} = \overline{\overline{AB}}$$



# NAND Gate (Static, Comp (Mos))

 


A	B	f
0	0	1
0	1	1
1	0	1
1	1	0



- Dual networks (Series  $\leftrightarrow$  parallel)
- Inverting logic
- AND logic? add inv to out
- N inp func  $\rightarrow 2^N$  tr

# Complex CMOS func

$$F = D + A \cdot (B + C)$$

 

# DC characteristics

  

(i)  $A = B : 0 \rightarrow 1$


(ii)  $A = 1, B : 0 \rightarrow 1$  (pull up weaker (i))

(iii)  $B = 1, A : 0 \rightarrow 1$  nmos not as strong as (ii)

$$V_t(M_1) = V_{t0}$$




$$V_t(M_2) = V_{t0} + \gamma \left( \sqrt{2\gamma_B + V_{int}} - \sqrt{2\gamma_B} \right)$$

# NAND: Propagation Delay

 


$$t_{pLH} = \begin{cases} A=B: 1 \rightarrow 0 \\ 0.69 \frac{R_p}{2} \cdot C_L \\ B=1, A: 1 \rightarrow 0 \quad (A \neq 1, B: 1 \rightarrow 0) \\ 0.69 R_p C_L \end{cases}$$

$$t_{pHL} = 0.69 \times 2 R_n C_L$$

   



# Simulation NAND

 

$t_{PLH}$

(i) $A=B: 1 \rightarrow 0$	fastest	35ps
(ii) $A=1, B=1 \rightarrow 0$	slowest	76ps
(iii) $B=1, A: 1 \rightarrow 0$		57ps

$t_{PHL}$

(i) $A=B: 0 \rightarrow 1$	slowest	69ps
(ii) $A=1, B: 0 \rightarrow 1$		62ps
(iii) $B=1, A: 0 \rightarrow 1$	fastest	50ps