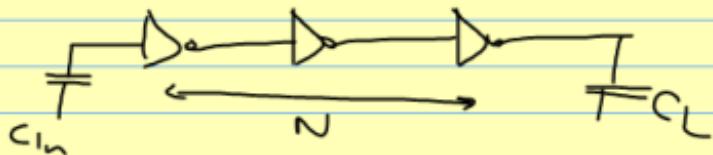


Inverter Chain Sizing Recap








$$F = \frac{C_L}{C_{in}} \quad F^* = \sqrt[N]{F}$$

$$\gamma = \frac{C_{int}}{C_g} \quad \text{for } \gamma=1 \quad f^* \approx 3.6$$

$$C_{int} \propto W$$


$$C_g \propto C_{ox} W$$

Logical Effort (P252)

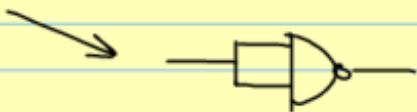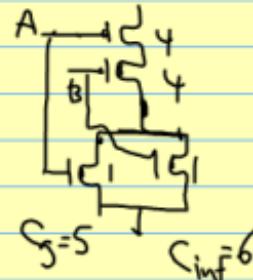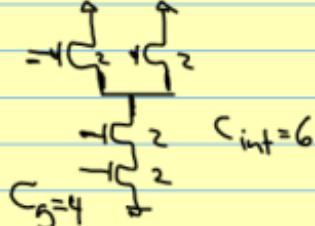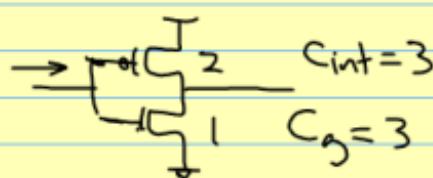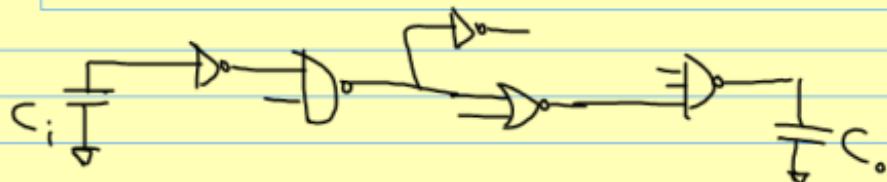

$C_o = 8 \quad C_{int} = 6$

Delay

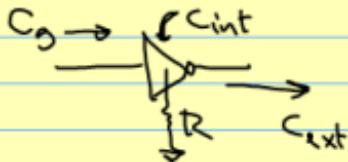

$$C_{int} = \gamma_{inv} C_g \rightarrow C_{ext}$$

$$\begin{aligned}
 t_p &= 0.69 R (C_{int} + C_{ext}) \\
 &= 0.69 R C_{int} \left(1 + \frac{C_{ext}}{C_{int}}\right) \\
 &= 0.69 R C_{int} \underbrace{\left(1 + \frac{C_{ext}}{\gamma_{inv} C_g}\right)}_{t_{inv,p}} \\
 &= t_{inv,p} \left(1 + \frac{1}{\gamma_{inv}} \cdot f\right) \rightarrow t_{inv,p} + \frac{t_{inv,p}}{\gamma_{inv}} \cdot f
 \end{aligned}$$

$$t_{f_{NAND}} = t_{NAND} + \frac{t_{NAND} \cdot f}{\gamma_{NAND}}$$

Normalize to $\text{inv}\phi$

$$\frac{t_{\text{inv}}}{t_{\text{inv}\phi}} = l + \frac{1}{\gamma_{\text{inv}}} f = p_{\text{inv}} + \frac{1}{\gamma_{\text{inv}}} g_{\text{inv}} f$$

$$\frac{t_{\text{hard}}}{t_{\text{inv}\phi}} = \frac{t_{\text{hard}\phi}}{t_{\text{inv}\phi}} + \frac{1}{\gamma_{\text{hard}}} \frac{t_{\text{hard}\phi}}{t_{\text{inv}\phi}} \cdot f$$

$$= \frac{t_{\text{hard}\phi}}{t_{\text{inv}\phi}} + \frac{1}{\gamma_{\text{inv}}} \frac{t_{\text{hard}\phi}/\gamma_{\text{hard}}}{t_{\text{inv}\phi}/\gamma_{\text{inv}}} \cdot f$$


$$= p_{\text{hard}} + \frac{1}{\gamma_{\text{inv}}} \cdot g_{\text{hard}} \cdot f$$

$$\frac{t_{\text{nor}}}{t_{\text{inv}\phi}} = p_{\text{nor}} + \frac{1}{\gamma_{\text{inv}}} g_{\text{nor}} \cdot f$$

Parasitic term P - Logical effort G

$$P_{inv} = 1$$
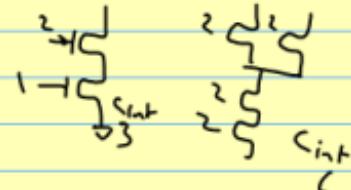
$$P_{nand} = \frac{t_{nand\phi}}{t_{inv\phi}} = \frac{(R C_{int})_{nand}}{(R C_{int})_{inv}}$$



$$= \frac{6}{3} = 2$$

$$P_{nor} = \frac{6}{3} = 2$$

Logical effort term

$$C_{int} = Y_c C_g$$


$$G_{inv} = 1 \quad G_{nand} = \frac{t_{nand\phi}/Y_{nand}}{t_{inv\phi}/Y_{inv}} = \frac{(R C_{int})_{nand}/Y_{nand}}{(R C_{int})_{inv}/Y_{inv}}$$

$$G_{nand} = \frac{(R C_g)_{nand}}{(R C_g)_{inv}} = 4/3$$

$$G_{nor} = 5/3$$


$$P_{AOI}, g_{AOI}$$

$$F = \overline{A \cdot B + C}$$

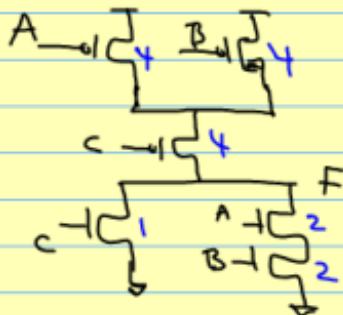

$$g_{AOI} = \begin{cases} 5/3 & C \\ 2 & A/B \end{cases}$$


$$P_{AOI} = 7/3$$

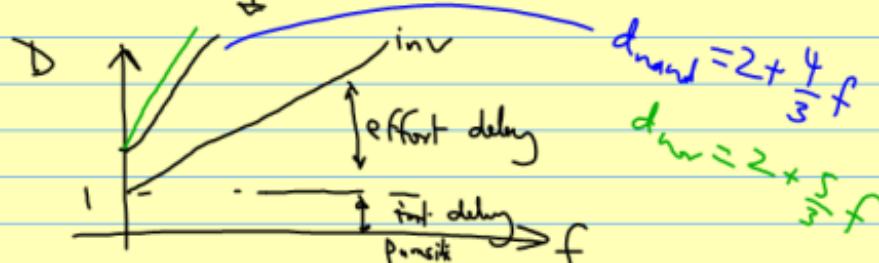

Optimal Sizes

$$d_x = p_x + g_x \frac{1}{\gamma_{inv}} f \xrightarrow{\frac{c_{j+1}}{c_j}}$$
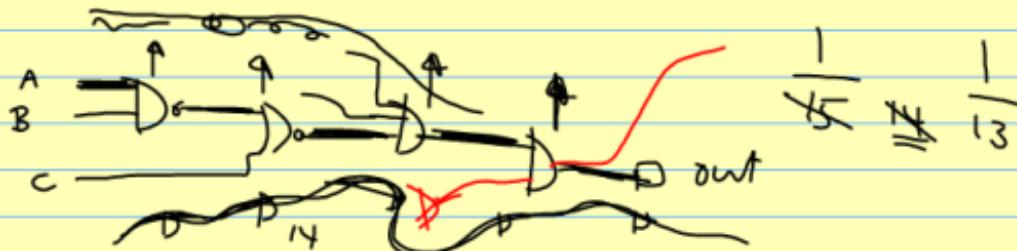
$$\begin{aligned} t_p &= t_{p_0} \cdot \sum_j \left(p_j + \frac{g_j}{\gamma_{inv}} \cdot f_j \right) \\ &= t_{p_0} \cdot \sum_j \left(p_j + \frac{g_j}{\gamma_{inv}} * \frac{c_{j+1}}{c_j} \right) \end{aligned}$$



Opt Size


$$\frac{\partial t_p}{\partial c_j} = t_p \left(\frac{g_j}{\gamma_{inv}} \left(-\frac{c_{j+1}}{c_j^2} \right) + \frac{g_{j-1}}{\gamma_{inv}} \frac{1}{c_{j-1}} \right) = 0$$

$$g_j \cdot \frac{c_{j+1}}{c_j} = g_{j-1} \cdot \frac{c_j}{c_{j-1}}$$

$$g_j \cdot f_j = g_{j-1} \cdot f_{j-1} = h^*$$

(rank effort)

Example

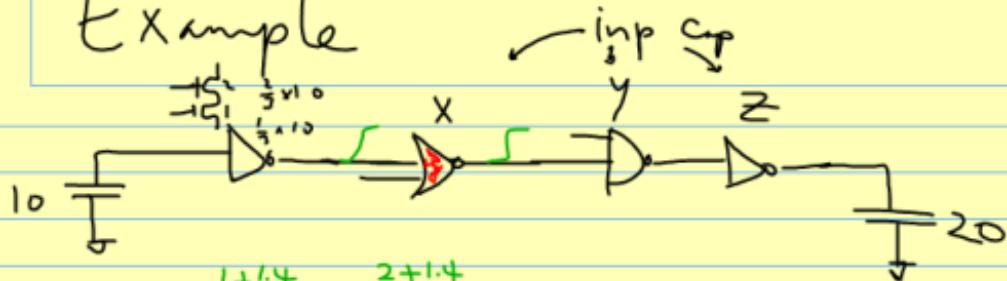

$$\mathfrak{P} = \begin{matrix} 1 & 2 & 2 & 1 \end{matrix}$$

$$\mathfrak{I} = \begin{matrix} 1 & \frac{5}{3} & \frac{4}{3} & 1 \end{matrix}$$

$$f = \begin{matrix} \frac{x}{1.0} & \frac{y}{x} & \frac{z}{y} & \frac{20}{z} \end{matrix} = h^*$$

$$h^* = \frac{x}{1.0} \cdot \frac{y}{x} \cdot \frac{2}{y} \cdot \frac{20}{z} \cdot \frac{5}{3} \cdot \frac{4}{3} = \frac{40}{9} \Rightarrow h^* = \sqrt[4]{\frac{40}{9}} \approx 1.4$$


Gate Sizing Example (Cont.)

$$1. \frac{x}{10} = h^* = 1.4 \Rightarrow x = 14$$

f




$$x = 14$$

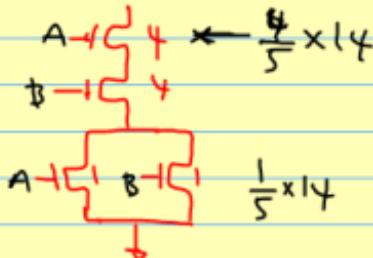


$$D = 6 + 1.4 \times 4 = \underline{11.6}$$

$$\frac{11.6}{5} = 2.32 F_{04}$$

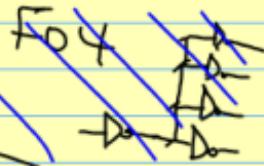

Branches

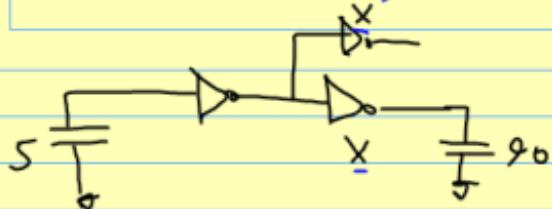

$$P = 1 \quad |$$

$$S = 1 \quad |$$

$$f = \frac{X}{5} \quad \frac{g_0}{X}$$

$$b = 2 \quad |$$

branching effort

$$\frac{C_{on-path} + C_{off-path}}{C_{on-path}}$$

branching Example (cont)

$$h^* = \sqrt{\frac{2}{5} \cdot g_0} = 6$$

$$\frac{2x}{5} = 6 \Rightarrow x = 15$$

$$D = (1+6) + (1+6) = 14$$

Method of Logical Effort

Vars on *PATH*

$$\textcircled{1} \quad G = \prod_j g_j \quad \text{path logical effort}$$


$$F = \prod_j f_j \quad \text{effective fanout}$$

$$B = \prod_j b_j \quad \text{branching effort}$$

$$H = GBF \quad \textcircled{2} \quad h^* = \sqrt[n]{H} = \prod_i b_i f_i^{\frac{c_{i+1}}{c_i}} \quad \textcircled{3}$$

$$\textcircled{4} \quad D = \sum_i p_i + \frac{N h^*}{f_{inv}}$$

Example

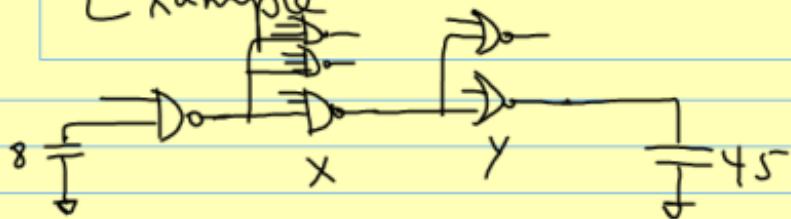

$$p = \underline{2} \quad \underline{3} \quad \underline{2}$$

$$g = \underline{\frac{4}{3}} \quad \frac{5}{3} \quad \frac{5}{3}$$

$$f = \frac{x}{8} \quad \frac{y}{x} \quad \frac{45}{7}$$

$$b = \underline{3} \quad \underline{2} \quad 1$$

$$H = \frac{4}{3} \times \frac{5}{3} \times \frac{5}{3} \times \underline{3} \times \underline{2} \times \frac{45}{8} = \underline{\frac{3}{5}}$$

$$h^* = \sqrt[3]{5^3} = 5$$

$$\underline{\frac{4}{3} \times \frac{x}{8} \times 3} = 5 \Rightarrow x = 10$$

$$D = \underline{7} + 3 \times 5 = 22$$

Example – 8-input AND

