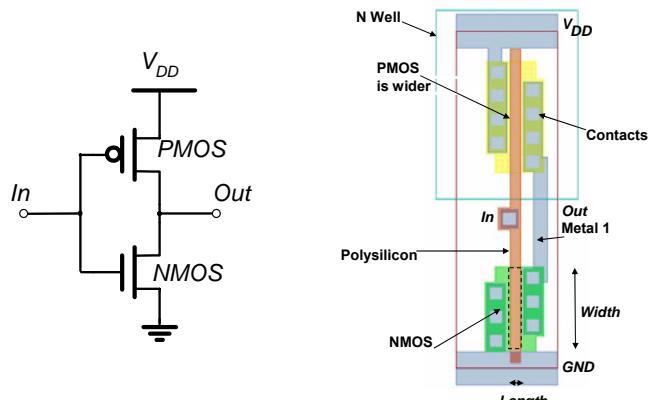



CMOS Inverter

Professor Chris H. Kim
 University of Minnesota
 Dept. of ECE
chriskim@umn.edu
www.umn.edu/~chriskim/


CMOS Inverter



The CMOS Inverter: A First Glance

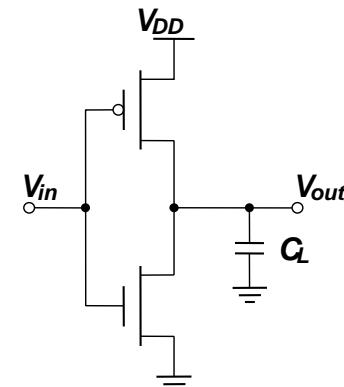

Two Inverters

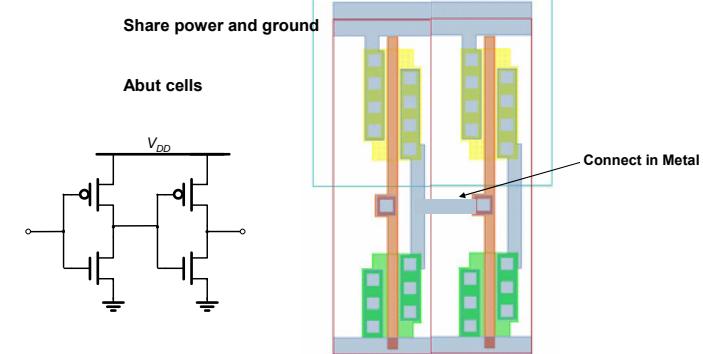


Voltage Transfer Characteristics



7


CMOS Inverter First-Order DC Analysis

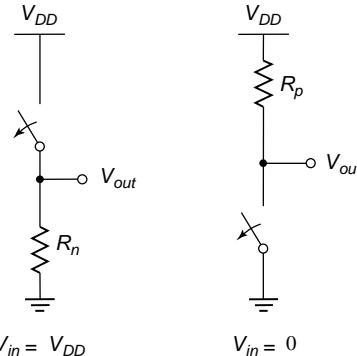

$$\begin{aligned}V_{OL} &= 0 \\V_{OH} &= V_{DD} \\V_M &= f(R_n, R_p)\end{aligned}$$


6

CMOS Inverter Load Characteristics

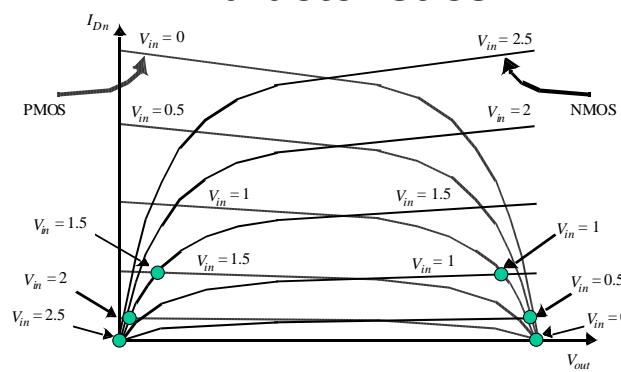


7

CMOS Inverter VTC

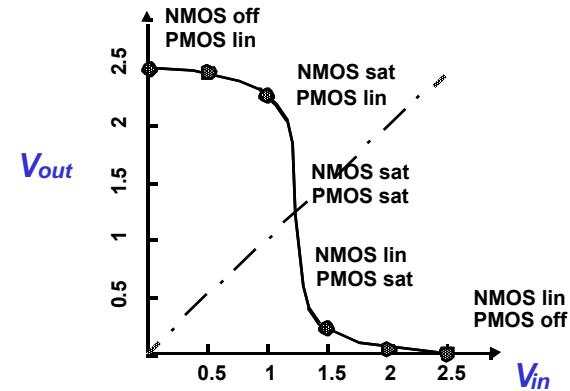


8

Simulated Inverter VTC (hspice)

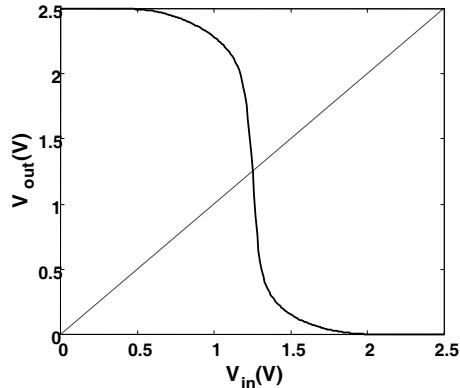


9

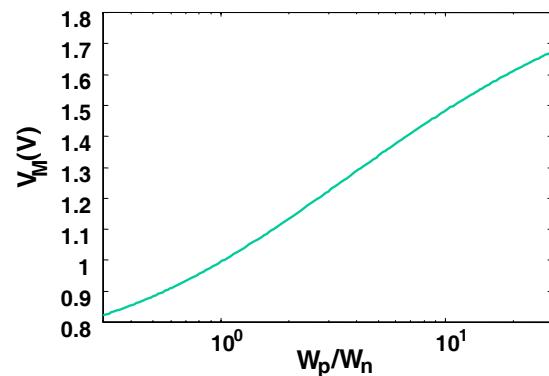Switching Threshold as a Function of Transistor Ratio




10

VTC as a function of VDD

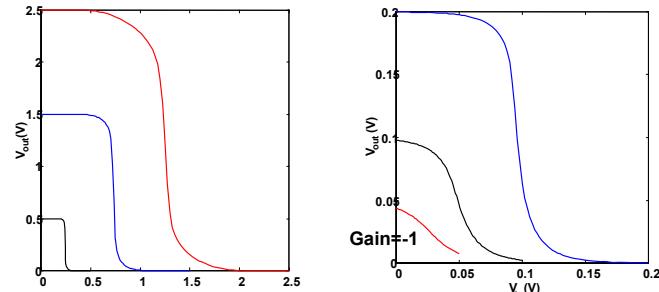


11

Impact of Sizing

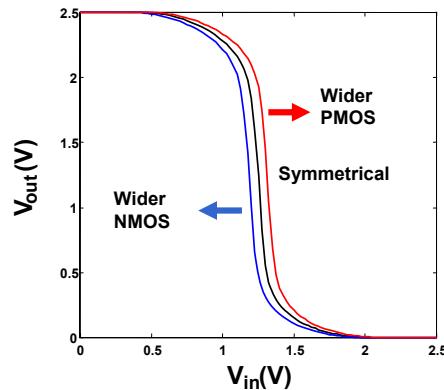


12

Impact of Process Variations

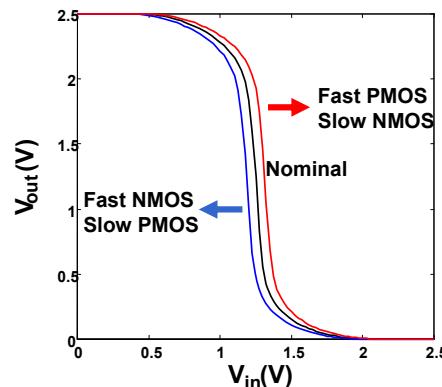


13

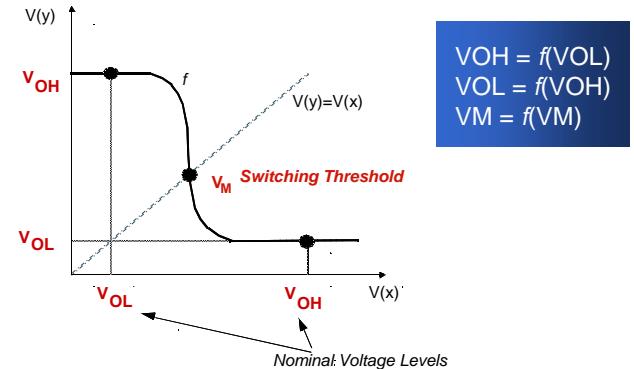DC Operation Voltage Transfer Characteristic




14

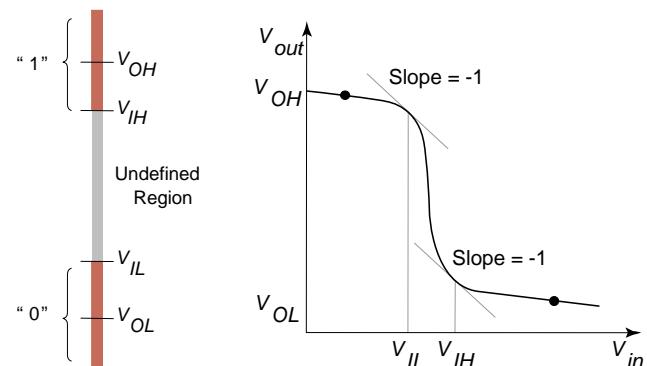Mapping between analog and digital signals



15

Definition of Noise Margins

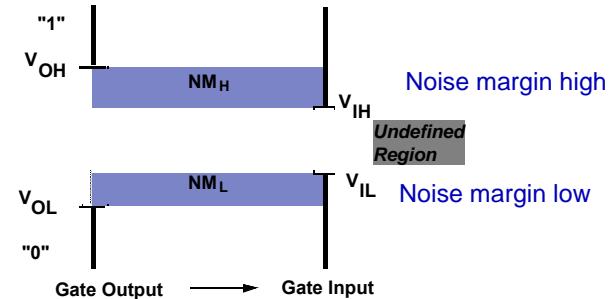


16

Example: CMOS Inverter DC Properties

- $V_{OH} = V_{DD} = 2.5V$
- $V_{OL} = 0V$
- $V_{IL} = 1.05V$
- $V_{IH} = 1.45V$
- $N_{MH} = 1.05V$
- $N_{ML} = 1.05V$
- $V_M = 1.2V$


17

Regenerative Property

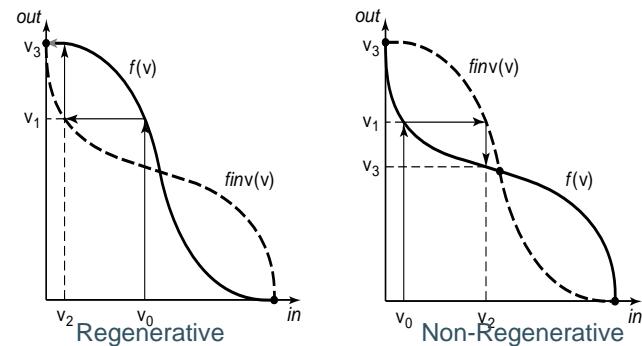


18

Regenerative Property

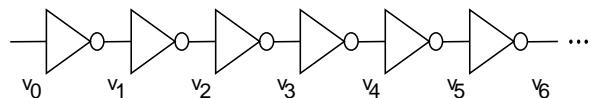

A chain of inverters

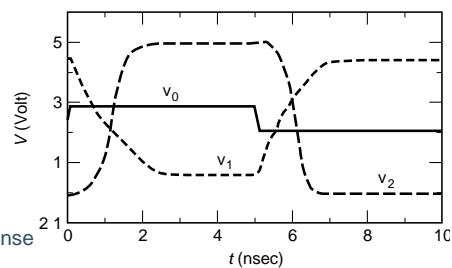


19

Propagation Delay




Computing the Capacitances

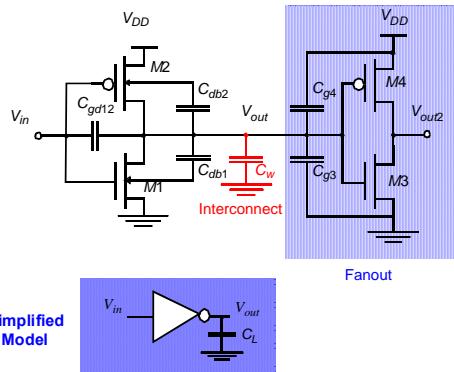

Simplified Model

21


CMOS Inverter: Transient Response

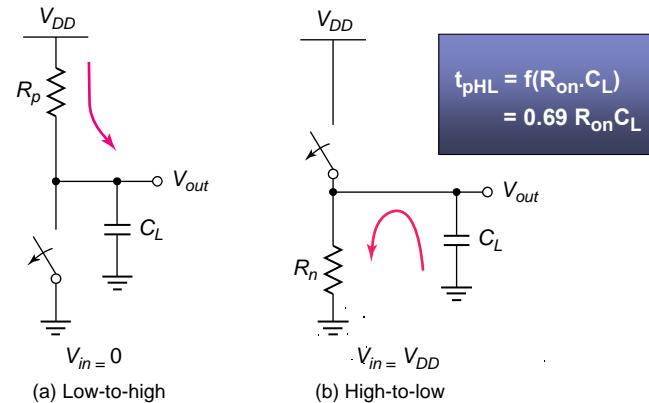

(b) High-to-low


22

Delay Definitions

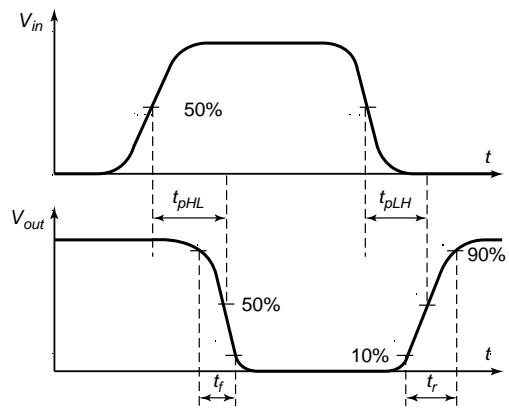


23

CMOS Inverter Propagation Delay

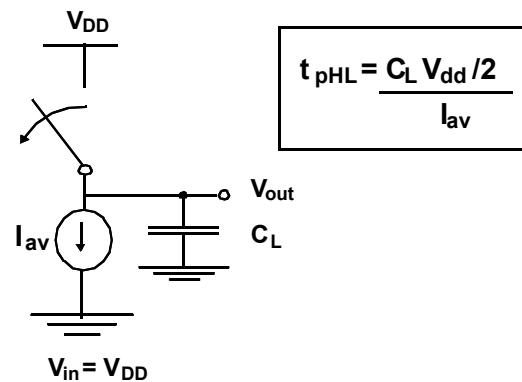

24

Transient Response

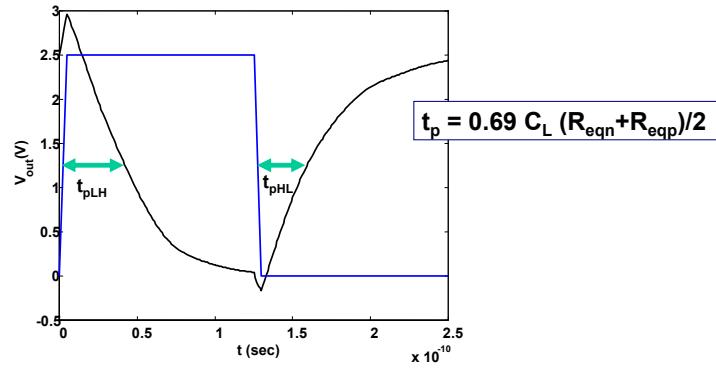


25

Design for Performance

- Keep capacitances small
- Increase transistor sizes
 - watch out for self-loading!
- Increase V_{DD}


26

Delay as a function of V_{DD}

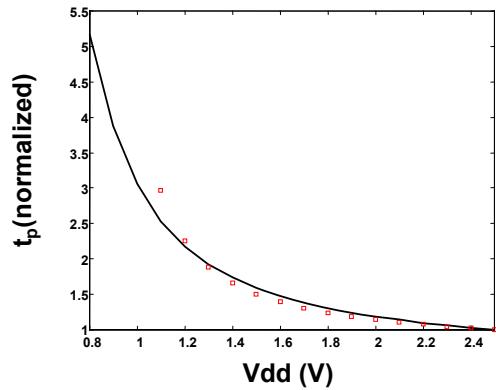


27

Device Sizing

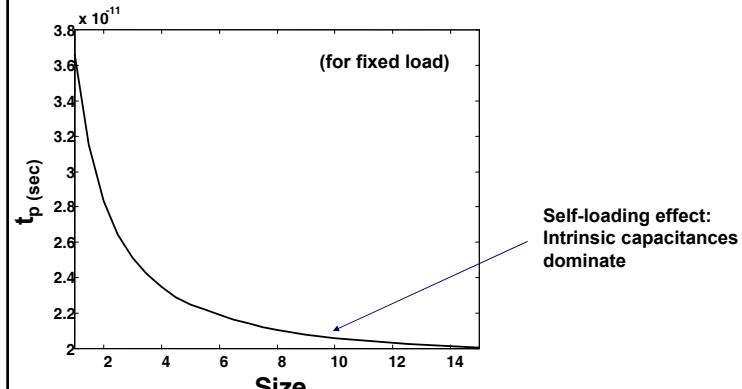


28

NMOS/PMOS ratio

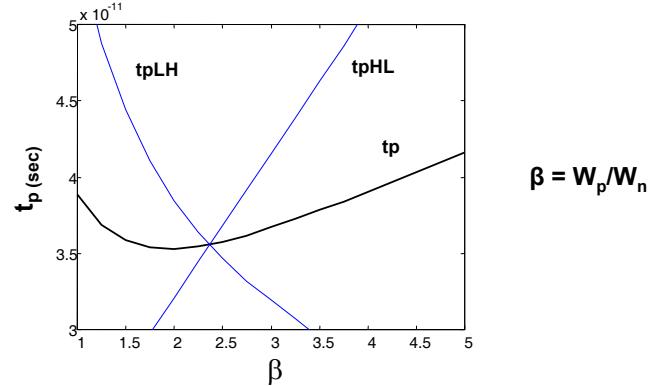

29


Impact of Rise Time on Delay

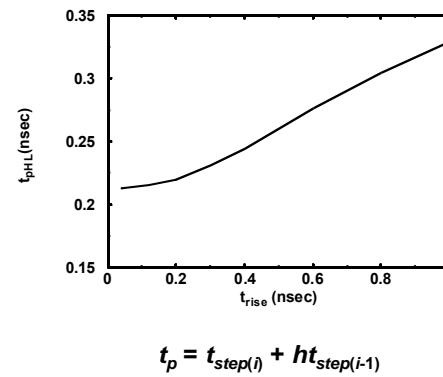

$$t_p = t_{step(i)} + h t_{step(i-1)}$$


30

Fan-in and Fan-out

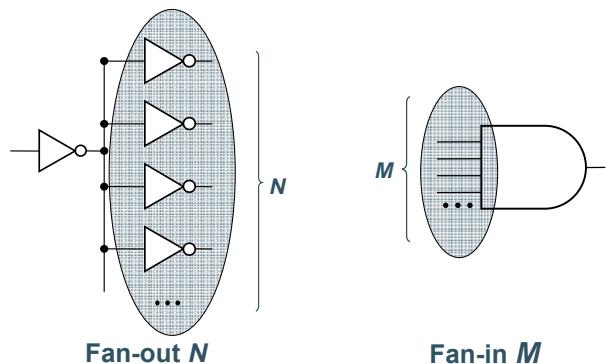

31

Ring Oscillator

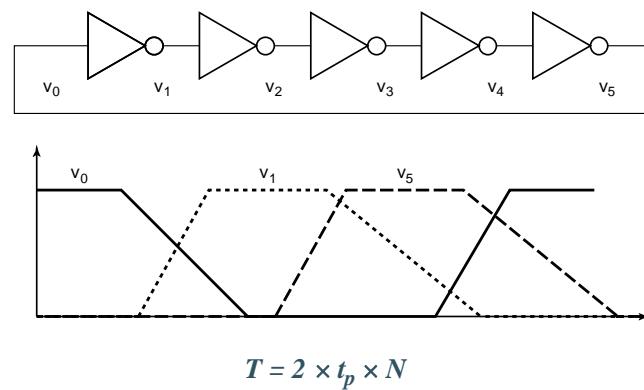

32

CMOS Properties

- Full rail-to-rail swing
- Symmetrical VTC
- Propagation delay function of load capacitance and resistance of transistors
- No static power dissipation (ignoring leakage current)
- Direct path current during switching