

# CMOS Inverter: Power Dissipation and Sizing

Professor Chris H. Kim

University of Minnesota  
Dept. of ECE

chriskim@umn.edu

# CMOS Inverter Power Dissipation




# Where Does Power Go in CMOS?

- **Switching power**
  - Charging capacitors
- **Leakage power**
  - Transistors are imperfect switches
- **Short-circuit power**
  - Both pull-up and pull-down on during transition
- **Static currents**
  - Biasing currents, in e.g. memory

3

# Dynamic Power Consumption

 


$$E_{0 \rightarrow 1} = \int_0^T P_{DD}(t) dt = V_{DD} \int_0^T i_{DD}(t) dt = V_{DD} \int_0^{V_{DD}} C_L dv_{out} = C_L V_{DD}^2$$

$$E_C = \int_0^T P_C(t) dt = \int_0^T v_{out} i_L(t) dt = \int_0^{V_{DD}} C_L v_{out} dv_{out} = \frac{1}{2} C_L V_{DD}^2$$

4


## Dynamic Power Consumption

 

- One half of the energy from the supply is consumed in the pull-up network and one half is stored on  $C_L$
- Energy from  $C_L$  is dumped during the 1→0 transition

5

## Circuits with Reduced Swing

 

$$E_{0 \rightarrow 1} = C_L V_{DD} (V_{DD} - V_{Th})$$

6

## Dynamic Power Consumption

Power = Energy/transition • Transition rate

$$= C_L V_{DD}^2 \cdot f_{0 \rightarrow 1}$$

$$= C_L V_{DD}^2 \cdot f \cdot P_{0 \rightarrow 1}$$

$$= C_{switched} V_{DD}^2 \cdot f$$

- Power dissipation is data dependent – depends on the switching probability
- Switched capacitance  $C_{switched} = C_L \cdot P_{0 \rightarrow 1}$

7

## Transition Activity and Power

- Energy consumed in  $N$  cycles,  $E_N$ :

$$E_N = C_L \cdot V_{DD}^2 \cdot n_{0 \rightarrow 1}$$

$n_{0 \rightarrow 1}$  – number of 0→1 transitions in  $N$  cycles


$$P_{avg} = \lim_{N \rightarrow \infty} \frac{E_N}{N} \cdot f = \left( \lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N} \right) \cdot C_L \cdot V_{DD}^2 \cdot f$$

$$\alpha_{0 \rightarrow 1} = \lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N} \cdot f$$

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{DD}^2 \cdot f$$

8


## Short Circuit Current

 


- Short circuit current is usually well controlled
 
## Transistor Leakage

- Transistors that are supposed to be off - leak



## Diode Leakage

 


$$I_{DL} = J_S \times A$$

$J_S = 10-100$  pA/mm<sup>2</sup> at 25 deg C for 0.25um CMOS  
 $J_S$  doubles for every 9 deg C!  
 Much smaller than transistor leakage in deep submicron

## Sizing of an Inverter Chain



## Inverter Chain

 


If  $C_L$  is given:

- How many stages are needed to minimize the delay?
  - How to size the inverters?
- May need some additional constraints.

13
 
## Inverter Delay

- Minimum length devices,  $L=0.25\mu\text{m}$
- Assume that for  $W_P = 2W_N = 2W$ 
  - same pull-up and pull-down currents
  - approx. equal resistances  $R_N = R_P$
  - approx. equal rise  $t_{pLH}$  and fall  $t_{pHL}$  delays
- Analyze as an RC network




$$R_P = R_{unit} \left( \frac{W_P}{W_{unit}} \right)^{-1} \approx R_{unit} \left( \frac{W_N}{W_{unit}} \right)^{-1} = R_N = R_W$$

$$\text{Delay (D): } t_{pHL} = (\ln 2) R_N C_L \quad t_{pLH} = (\ln 2) R_P C_L$$

$$\text{Load for the next stage: } C_{gin} = 3 \frac{W}{W_{unit}} C_{unit}$$

14

## Inverter with Load

 


$k$  is a constant, equal to 0.69 for step input

Assumptions: no load  $\rightarrow$  zero delay

$$W_{unit} = 1$$

15

## Inverter with Load

 

$$\begin{aligned} \text{Delay} &= kR_W(C_{int} + C_L) = kR_W C_{int} + kR_W C_L = kR_W C_{int} (1 + C_L / C_{int}) \\ &= \text{Delay (Intrinsic)} + \text{Delay (Load)} \end{aligned}$$

16

## Delay Formula


$$\text{Delay} \sim R_W (C_{int} + C_L)$$

$$t_p = kR_W C_{int} (1 + C_L / C_{int}) = t_{p0} (1 + f / \gamma)$$

$$\begin{aligned} C_{int} &= \gamma C_{gin} \text{ with } \gamma \approx 1 \\ f &= C_L / C_{gin} - \text{effective fanout} \\ R &= R_{unit} / W ; C_{int} = WC_{unit} \\ t_{p0} &= 0.69 R_{unit} C_{unit} \end{aligned}$$

17

## Apply to Inverter Chain

 

$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

$$t_{pj} \sim R_{unit} C_{unit} \left( 1 + \frac{C_{gin,j+1}}{C_{gin,j}} \right) \quad \boxed{\gamma = 1}$$

$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{i=1}^N \left( 1 + \frac{C_{gin,j+1}}{C_{gin,j}} \right), \quad C_{gin,N+1} = C_L$$

18

## Optimal Tapering for Given N

Delay equation has  $N - 1$  unknowns,  $C_{gin,2} - C_{gin,N}$

Minimize the delay, find  $N - 1$  partial derivatives

$$\text{Result: } C_{gin,j+1} / C_{gin,j} = C_{gin,j} / C_{gin,j-1}$$

Size of each stage is the geometric mean of two neighbors

$$C_{gin,j} = \sqrt{C_{gin,j-1} C_{gin,j+1}}$$

- each stage has the same effective fanout ( $C_{out} / C_{in}$ )
- each stage has the same delay

19

## Optimum Delay and Number of Stages

When each stage is sized by  $f$  and has same eff. fanout  $f$ :

$$f^N = F = C_L / C_{gin,1}$$

Effective fanout of each stage:


$$f = \sqrt[N]{F}$$

Minimum path delay

$$t_p = N t_{p0} \left( 1 + \sqrt[N]{F} \right)$$

20

## Example

 

$C_L/C_1$  has to be evenly distributed across  $N=3$  stages:

$$f = \sqrt[3]{8} = 2$$

21

## Optimum Number of Stages

For a given load,  $C_L$  and given input capacitance  $C_{in}$   
Find optimal number of stages,  $N$ , and optimal sizing,  $f$

$$C_L = F \cdot C_{in} = f^N C_{in} \text{ with } N = \frac{\ln F}{\ln f}$$

$$t_p = N t_{p0} (F^{1/N} / \gamma + 1) = \frac{t_{p0} \ln F}{\gamma} \left( \frac{f}{\ln f} + \frac{\gamma}{\ln f} \right)$$

$$\frac{\partial t_p}{\partial f} = \frac{t_{p0} \ln F}{\gamma} \cdot \frac{\ln f - 1 - \gamma/f}{\ln^2 f} = 0$$


For  $\gamma = 0$ ,  $f = e$ ,  $N = \ln F$   $f = \exp(1 + \gamma/f)$

22

## Optimum Effective Fanout $f$

Optimum  $f$  for given process defined by  $\gamma$

$$f = \exp(1 + \gamma/f)$$

 


$f_{opt} = 3.6$   
for  $\gamma=1$

23

## Impact of Loading on $t_p$

With self-loading  $\gamma=1$

 

24

## Normalized Delay Function of $F$


$$t_p = Nt_{p0} \left(1 + \sqrt[N]{F/\gamma}\right)$$

$$t_p = Nt_{p0} \left(1 + \sqrt[N]{F}\right), \text{ with } \gamma = 1$$

$F$	Unbuffered	Two Stage	Inverter Chain
10	11	8.3	8.3
100	101	22	16.5
1000	1001	65	24.8
10,000	10,001	202	33.1

25

## Buffer Design

 

26