Wires

Professor Chris Kim

University of Minnesota
Dept. of ECE

chriskim@umn.edu
www.umn.edu/~chriskim/

Wire Models

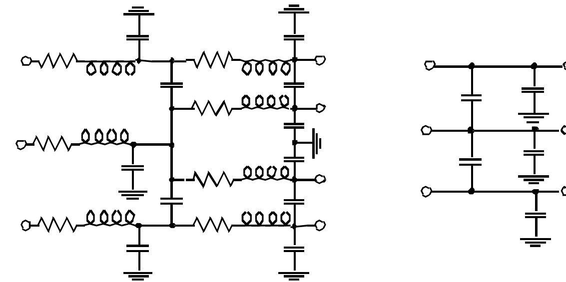

All-inclusive model

Capacitance-only

INTERCONNECT

Capacitance of Wire Interconnect

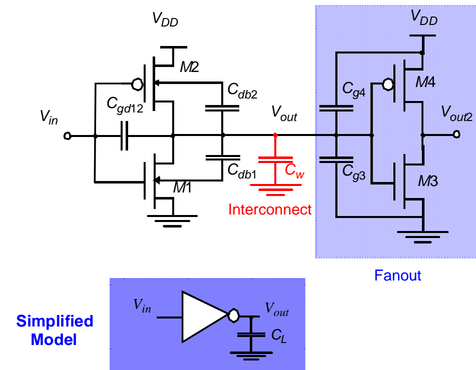

Capacitance: The Parallel Plate Model

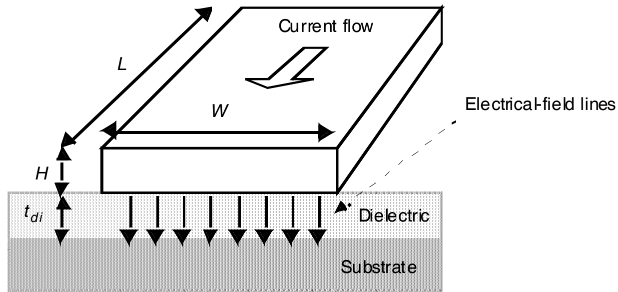

$$c_{int} = \frac{\varepsilon_{di}}{t_{di}} WL \qquad S_{C_{wire}} = \frac{S}{S \cdot S_L} = \frac{1}{S_L}$$

Permittivity

Material	ε_r
Free space	1
Aerogels	~1.5
Polyimides (organic)	3-4
Silicon dioxide	3.9
Glass-epoxy (PC board)	5
Silicon Nitride (Si_3N_4)	7.5
Alumina (package)	9.5
Silicon	11.7

Fringing Capacitance

$$c_{wire} = c_{pp} + c_{fringe} = \frac{w\varepsilon_{di}}{t_{di}} + \frac{2\pi\varepsilon_{di}}{\log(t_{di}/H)}$$

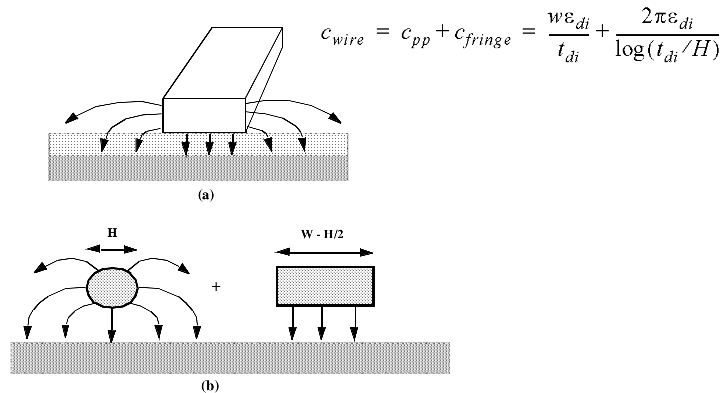

Fringing versus Parallel Plate

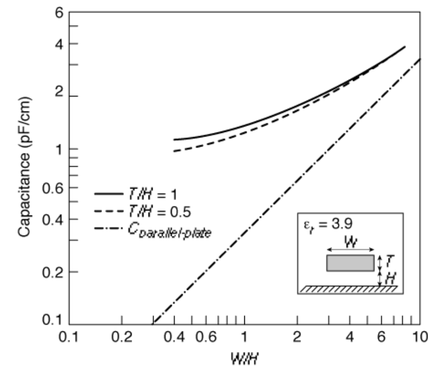

(from [Bakoglu89])

Interwire Capacitance

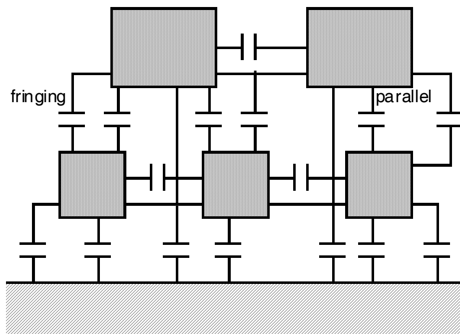

Impact of Interwire Capacitance

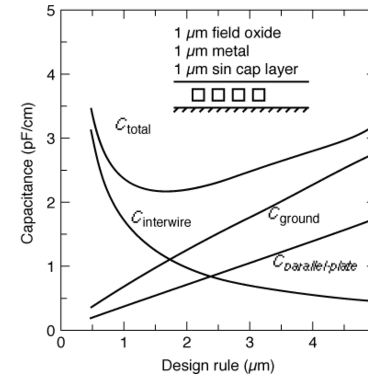

(from [Bakoglu89])

Wiring Capacitances (0.25 μm CMOS)

	Field	Active	Poly	Al1	Al2	Al3	Al4
Poly	88						
	54						
Al1	30	41	57				
	40	47	54				
Al2	13	15	17	36			
	25	27	29	45			
Al3	8.9	9.4	10	15	41		
	18	19	20	27	49		
Al4	6.5	6.8	7	8.9	15	35	
	14	15	15	18	27	45	
Al5	5.2	5.4	5.4	6.6	9.1	14	38
	12	12	12	14	19	27	52

INTERCONNECT

Resistance

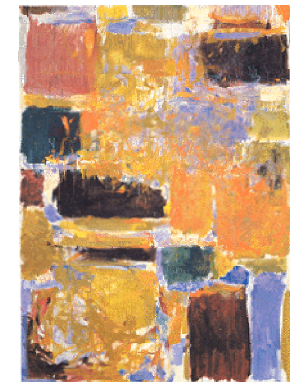

Wire Resistance

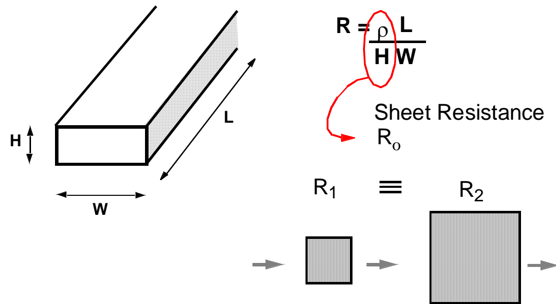

Interconnect Resistance

Material	ρ (Ω-m)
Silver (Ag)	1.6×10^{-8}
Copper (Cu)	1.7×10^{-8}
Gold (Au)	2.2×10^{-8}
Aluminum (Al)	2.7×10^{-8}
Tungsten (W)	5.5×10^{-8}

Dealing with Resistance

- **Selective Technology Scaling**
- **Use Better Interconnect Materials**
  - reduce average wire-length
  - e.g. copper, silicides
- **More Interconnect Layers**
  - reduce average wire-length

Polycide Gate MOSFET

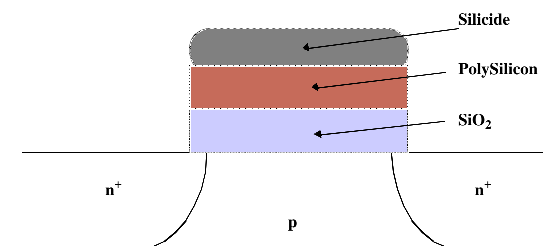

Silicides: WSi_2, $TiSi_2$, $PtSi_2$ and TaSi

Conductivity: 8-10 times better than Poly

Sheet Resistance

Material	Sheet Resistance (Ω/❑)
n- or p-well diffusion	1000 – 1500
n^+, p^+ diffusion	50 – 150
n^+, p^+ diffusion with silicide	3 – 5
n^+, p^+ polysilicon	150 – 200
n^+, p^+ polysilicon with silicide	4 – 5
Aluminum	0.05 – 0.1

Modern Interconnect

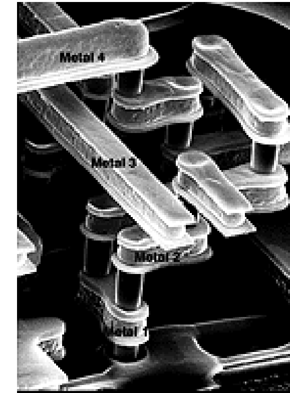

Example: Intel 0.25 micron Process

5 metal layers
Ti/Al - Cu/Ti/TiN
Polysilicon dielectric

LAYER	PITCH	THICK	A.R.
Isolation	0.67	0.40	-
Polysilicon	0.64	0.25	-
Metal 1	0.64	0.48	1.5
Metal 2	0.93	0.90	1.9
Metal 3	0.93	0.90	1.9
Metal 4	1.60	1.33	1.7
Metal 5	2.56	1.90	1.5
	µm	µm	

Layer pitch, thickness and aspect ratio

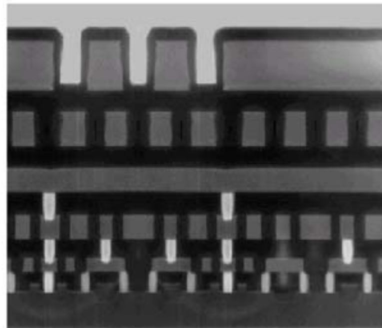

Modern Interconnect

- 90nm process

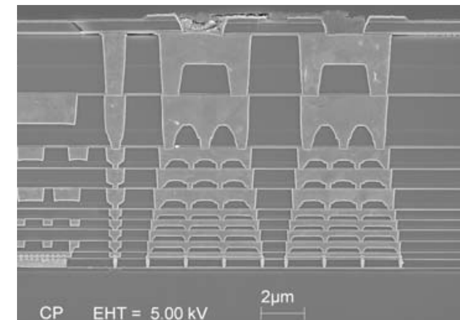

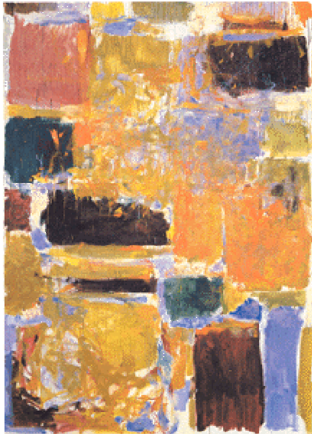

Interconnect Modeling

The Lumped Model

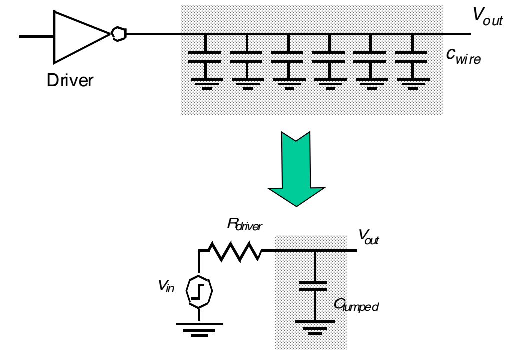

The Lumped RC-Model
The Elmore Delay

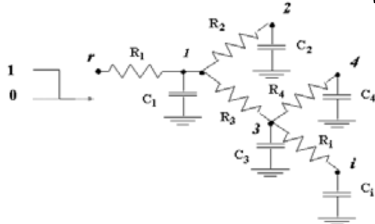

$$R_{ik} = \sum R_j \Rightarrow (R_j \in [path(s \to i) \cap path(s \to k)])$$

$$\tau_{Di} = \sum_{k=1}^{N} C_k R_{ik}$$

The Elmore Delay: RC Chain

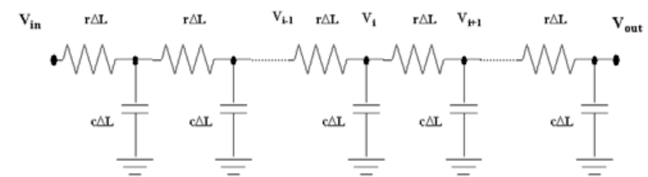

$$\tau_N = \sum_{i=1}^{N} R_i \sum_{j=i}^{N} C_j = \sum_{i=1}^{N} C_i \sum_{j=1}^{i} R_j$$

Wire Model

Assume: Wire modeled by N equal-length segments

$$\tau_{DN} = \left(\frac{L}{N}\right)^2 (rc + 2rc + \ldots + Nrc) = (rcL^2)\frac{N(N+1)}{2N^2} = RC\frac{N+1}{2N}$$

For large values of N:

$$\tau_{DN} = \frac{RC}{2} = \frac{rcL^2}{2}$$

The Distributed RC-line

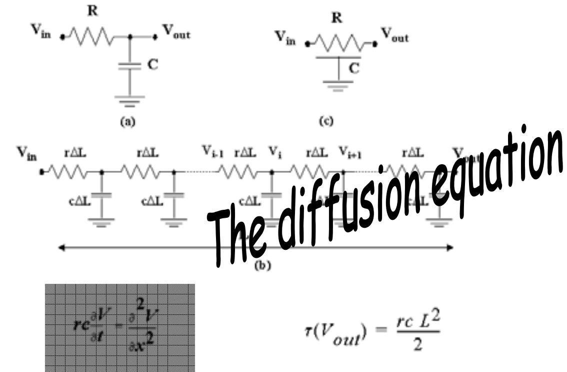

Step-response of RC wire as a function of time and space

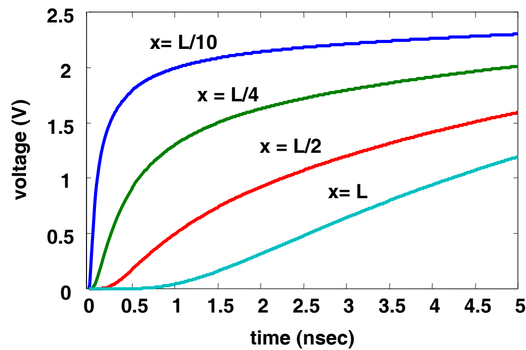

RC-Models

Voltage Range	Lumped RC-network	Distributed RC-network
0→50% (t_p)	0.69 RC	0.38 RC
0→63% (τ)	RC	0.5 RC
10%→90% (t_r)	2.2 RC	0.9 RC

Step Response of Lumped and Distributed RC Networks: Points of Interest.

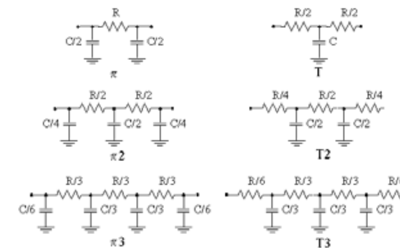

Driving an RC-line

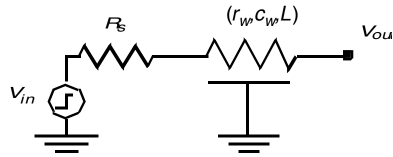

$$\tau_D = R_s C_w + \frac{R_w C_w}{2} = R_s C_w + 0.5 r_w c_w L^2$$

$$t_p = 0.69 R_s C_w + 0.38 R_w C_w$$